

### 13. Band-Pass Report 40 kHz (and PLL check)

UFO Doctor, Dec. 20th, 2011, rev. Jan 18<sup>th</sup>, 2012

V1.2

### 1. Simulation and Experiment

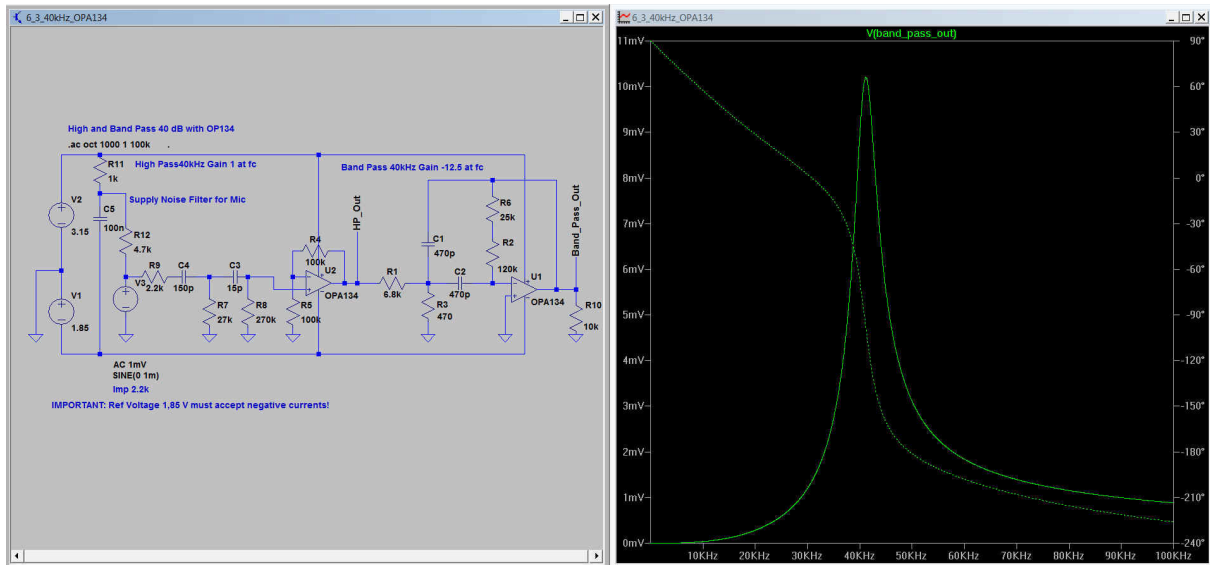


Fig. 1. Simulation V5 dual HP and single BP at 1 to 100kHz, Gain 12 at fc with OPA2134

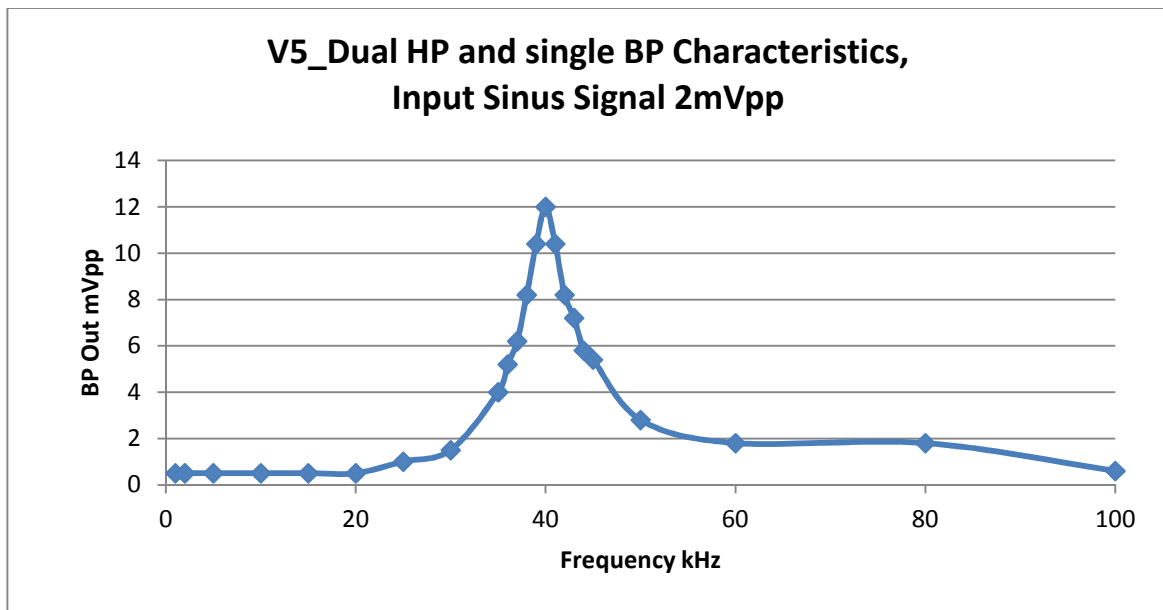


Fig.2. Experimental result with OPA2134 (10MHz, low noise) Input Voltage: 2 mVpp, output max. 12mVpp

### 2. Discussion

Calculation, Simulation and Experiment match together. The OPAMP should show a bandwidth-product of about 10 MHz and not too much noise. The low-cost Opamp MCP6022 might be sufficient.

### 3. Experiment with same circuit, but with MCP6022

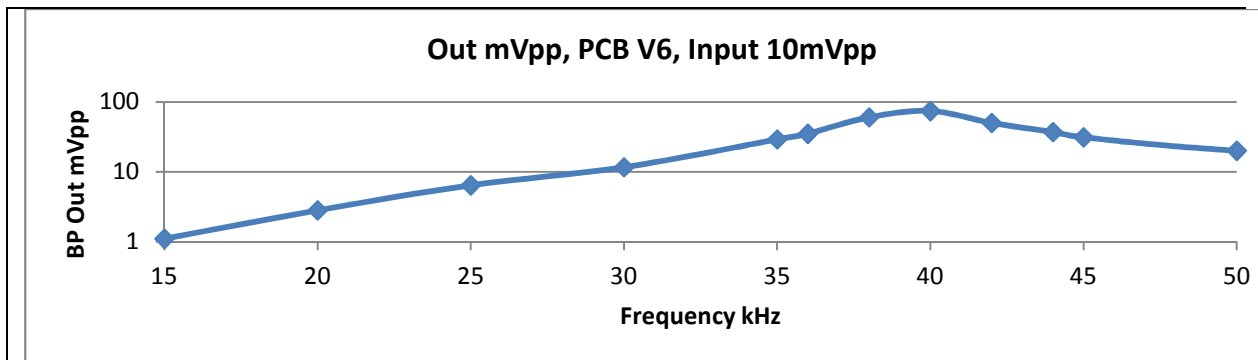


Fig.3. Experimental result with MCP6022 (10MHz, low cost)  
Input Voltage: 10 mVpp, output max. 90 mVpp, Gain not perfect but ok  
Noise: about 1 mVpp

#### Additional Info:

R1: 10E

R2: removed (no electret Mic!)

Cx parallel to R5: 100pF (oscillating without?)

R12: 470k

C12: 22pF

Total current consumption at 5V: 8 mA

Voltage loss at R1: 17 mV for MCP6022

### 4. PLL Behavior 18. Jan, 2012

Lower lock in: 38.5 kHz

f1: 39.9 kHz

f2: 40.2 kHz

Upper lock in: 41.9kHz

Just perfect for FSK with +/- 2% frequency deviation!