

UFO-Doctor, Febr. 25th, 2015

1. Introduction

The IR-LED SFH 4233 needs >1.4V@1A (max 1.8@1A), see datasheet.

Three such IR-Diodes in series require a voltage > 5.4V and should be driven by current control.

Our supply is a two cell Lipo 0.9Ah, nominal voltage 7.4V, fully charged 8.4V and 6.4V almost empty.

Thus, it make sense to apply a switched step-down converter, delivering a constant output voltage of about 6 V/1A during all Lipo charging conditions for constant operation.

2. Circuit

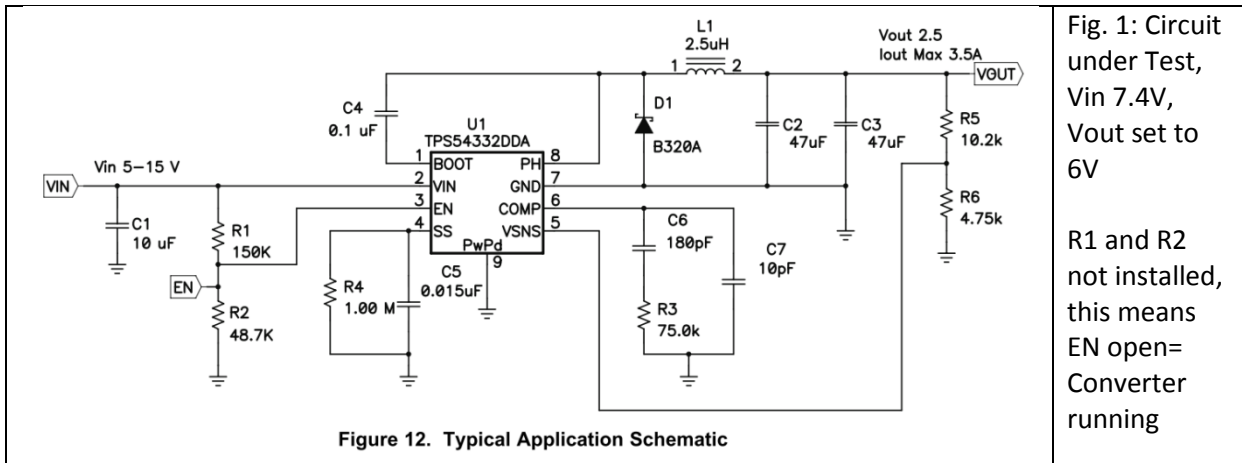


Fig. 1: Circuit under Test, Vin 7.4V, Vout set to 6V

R1 and R2 not installed, this means EN open= Converter running

3. Problem

The step-down converter TPS54332 (according to the application note) is quite fine, but shows in practice oscillations at little load and low input supply voltage.

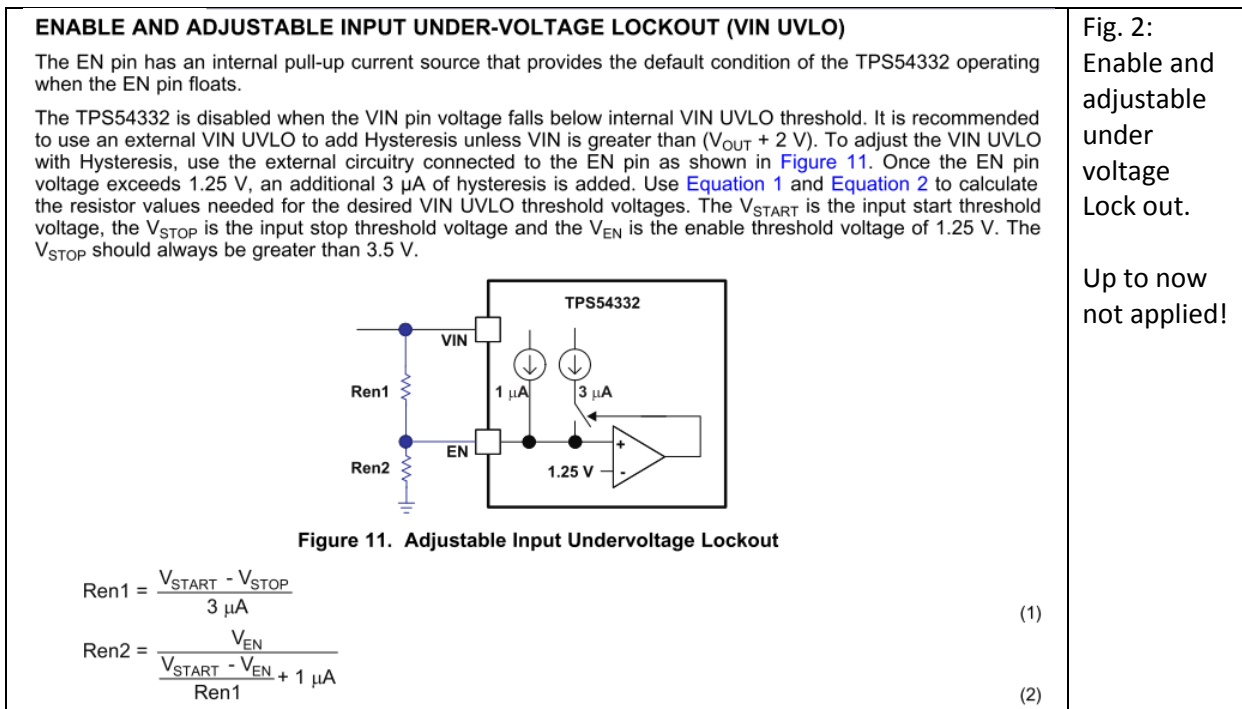
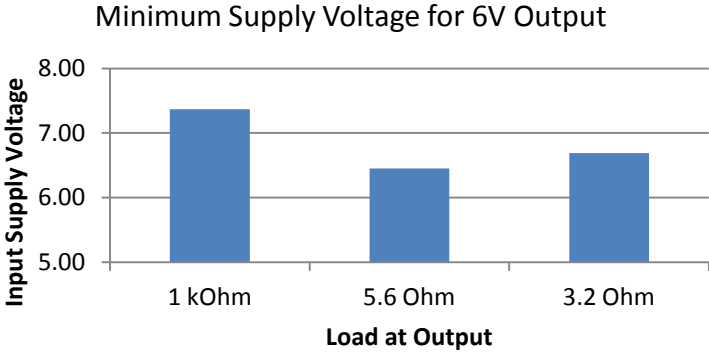
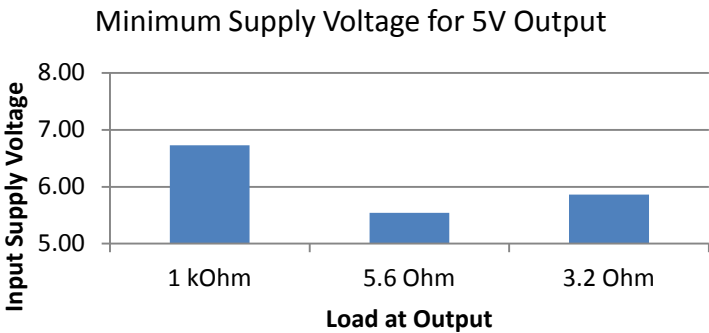


Fig. 2: Enable and adjustable under voltage Lock out.

Up to now not applied!

## 4. Experimental results


### 4.1. Minimum Supply Voltage

 <p>Minimum Supply Voltage for 6V Output</p> <table border="1"> <thead> <tr> <th>Load at Output</th> <th>Input Supply Voltage</th> </tr> </thead> <tbody> <tr> <td>1 kOhm</td> <td>~7.4</td> </tr> <tr> <td>5.6 Ohm</td> <td>~6.5</td> </tr> <tr> <td>3.2 Ohm</td> <td>~6.7</td> </tr> </tbody> </table>	Load at Output	Input Supply Voltage	1 kOhm	~7.4	5.6 Ohm	~6.5	3.2 Ohm	~6.7	<p>Fig. 3: Minimum Supply Voltage for 6V output at different loads</p>
Load at Output	Input Supply Voltage								
1 kOhm	~7.4								
5.6 Ohm	~6.5								
3.2 Ohm	~6.7								
 <p>Minimum Supply Voltage for 5V Output</p> <table border="1"> <thead> <tr> <th>Load at Output</th> <th>Input Supply Voltage</th> </tr> </thead> <tbody> <tr> <td>1 kOhm</td> <td>~6.8</td> </tr> <tr> <td>5.6 Ohm</td> <td>~5.5</td> </tr> <tr> <td>3.2 Ohm</td> <td>~5.9</td> </tr> </tbody> </table>	Load at Output	Input Supply Voltage	1 kOhm	~6.8	5.6 Ohm	~5.5	3.2 Ohm	~5.9	<p>Fig. 4: Minimum Supply Voltage for 5V output at different loads</p>
Load at Output	Input Supply Voltage								
1 kOhm	~6.8								
5.6 Ohm	~5.5								
3.2 Ohm	~5.9								

Comment:

The output voltage of the step-down converter should be set to maximum 5V for proper operation at variable Lipo supply voltages from 8.4V to 6.4V.

### 4.2. DC-DC Conversion Efficiency

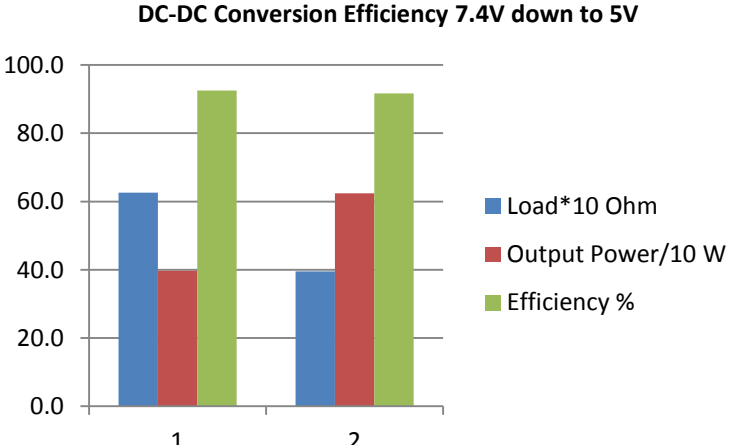 <p>DC-DC Conversion Efficiency 7.4V down to 5V</p> <table border="1"> <thead> <tr> <th>Condition</th> <th>Load*10 Ohm</th> <th>Output Power/10 W</th> <th>Efficiency %</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>~62</td> <td>~40</td> <td>~92</td> </tr> <tr> <td>2</td> <td>~40</td> <td>~62</td> <td>~92</td> </tr> </tbody> </table>	Condition	Load*10 Ohm	Output Power/10 W	Efficiency %	1	~62	~40	~92	2	~40	~62	~92	<p>Fig. 5: Conversion Efficiency</p> <p>Comment: The DC-DC Step Down Conversion for heavy loads (about 6 and 4 Ohm) is very efficient, more than 90%!</p>
Condition	Load*10 Ohm	Output Power/10 W	Efficiency %										
1	~62	~40	~92										
2	~40	~62	~92										

## 5. Conclusion

It make sense to convert the variable input supply from the Lipo (8.4V to 6.4V) down to 5V for a constant voltage for the high-power IR-LED, consuming 2x1A peak.